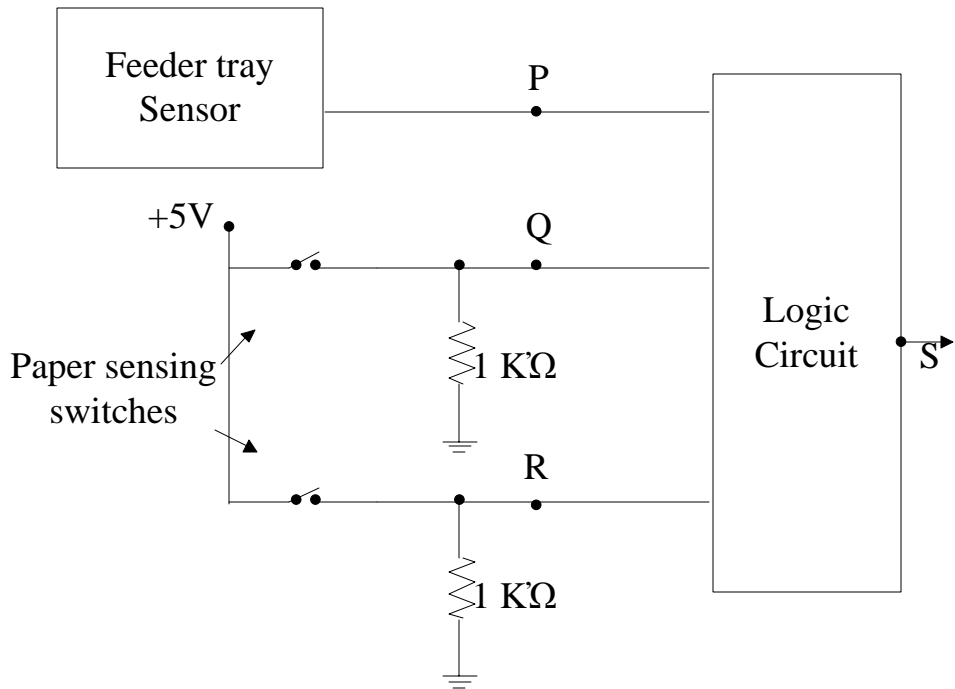


Following figure is a simple copy machine. A stop signal S is to be generated to stop the machine operation and energize an indicator light whenever either of the following conditions exists:

- i) There is no paper in the paper feeder tray
- ii) The two micro-switches in the paper path are activated, indicating a jam in the paper path.

The presence of paper in the feeder tray is indicated by a HIGH at logic signal P. Each of the micro switches produces a logic signal (Q & R) that goes HIGH whenever paper is passing over the switch to activate it. Design a logic circuit to produce a HIGH at output signal S for the stated conditions.



**Solution:**

The S output will be a logic 1 whenever P=0 because this indicates no paper in the paper feeder tray. S will also be a 1 for the two cases where Q and R both indicating a paper jam.

1. Truth Table :

Inputs			Output
P	Q	R	S
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

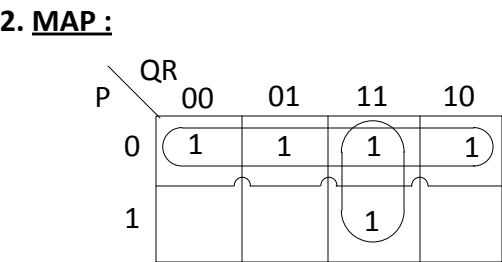


Fig: Map for S

$$S = P' + QR$$

**3. Circuit Diagram :**

